

Modelling Guitar Effects: Transient, Non-linear Circuit Solver

Johnathon Caguiat, Philip Christian, Steven Dong, Ciaran Geaney

ECE1254 Final Project

April 20th, 2016

Overview

- Objective and Background: Transience with Non-linearity
- Variable Time-stepping
- Diodes and Transistors: Equations, Stamps and Testing
- Modelling of Guitar effects and Insights Gained

Objective

- Create a circuit solver which can solve a system transience and nonlinearity.
- System of choice: guitar sound modulation.
 - Sound is a transient input voltage input
 - Additional transience and non-linearity can be added by choosing relevant circuit elements: capacitors, diodes and transistors

Adding Non-Linear Elements to Transient Systems

$$\begin{cases} Gx(t) + C\dot{x}(t) + \mathbf{F}'(\mathbf{x}) = Bu(t) \\ y(t) = L^T x(t) \end{cases} \quad \begin{cases} Gx(t) + C\dot{x}(t) + \mathbf{H}\mathbf{g}(\mathbf{x}) = Bu(t) \\ y(t) = L^T x(t) \end{cases}$$

Example of how these might look for a two connection, non-linear resistor:

$$\begin{array}{c} \mathbf{F}'(\mathbf{x}) \\ \begin{matrix} n1 \\ n2 \end{matrix} \begin{bmatrix} 1 \\ \vdots \\ g \\ \vdots \\ -g \\ \vdots \end{bmatrix} \end{array} \quad \longleftrightarrow \quad \begin{array}{cc} \mathbf{H} & \mathbf{g}(\mathbf{x}) \\ n^* & 1 \\ \begin{matrix} n1 \\ n2 \end{matrix} \begin{bmatrix} \vdots \\ 1 \\ \vdots \\ \vdots \\ -1 \\ \vdots \end{bmatrix} & n^* \begin{bmatrix} \vdots \\ g \\ \vdots \end{bmatrix} \end{array}$$

Implementing Trapezoidal Rule

Add two x_{n+1} and x_n such that we can use an approximation for the first derivative:

$$\begin{array}{r} Gx_{n+1} + C\dot{x}_{n+1} + F'(x_{n+1}) = Bu_{n+1} \\ + \quad Gx_n + C\dot{x}_n + F'(x_n) = Bu_n \\ \hline \end{array}$$


$$G(x_{n+1} + x_n) + C(x_{n+1} + x_n) + F'(x_{n+1}) + F'(x_n) = B(u_{n+1} + u_n)$$

Substitute the approximation of the : $\frac{x_{n+1} - x_n}{\Delta t} = \frac{\dot{x}_{n+1} + \dot{x}_n}{2}$

$$G(x_{n+1} + x_n) + 2C\left(\frac{x_{n+1} - x_n}{\Delta t}\right) + F'(x_{n+1}) + F'(x_n) = B(u_{n+1} + u_n)$$

Implementing Trapezoidal Rule

Collect x terms and divide by 2:
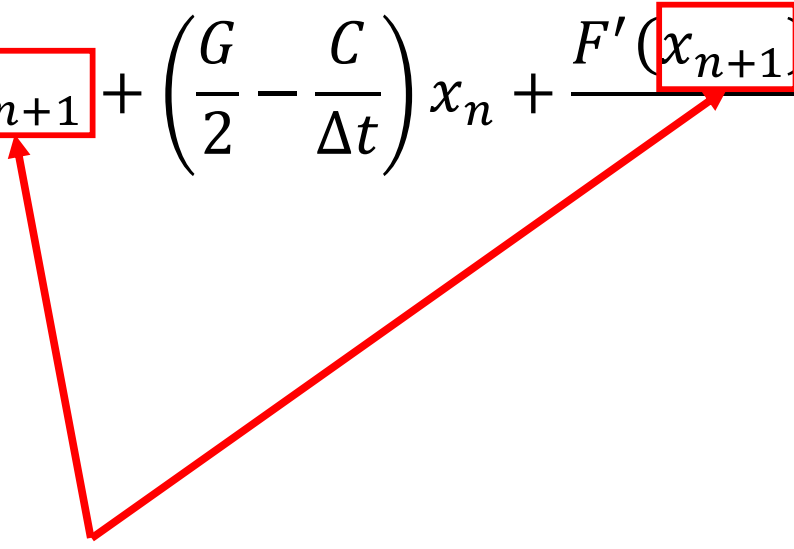
$$\left(\frac{G}{2} + \frac{C}{\Delta t}\right) x_{n+1} + \left(\frac{G}{2} - \frac{C}{\Delta t}\right) x_n + \frac{F'(x_{n+1}) + F'(x_n)}{2} = \frac{B(u_{n+1} + u_n)}{2}$$


x_{n+1} is now non-linear and requires Newton's Method to solve for each time step

Implementing Newton's Method

Recall Newton's Method:


$$x_{k+1} = x_k - [J(F(x_k))]^{-1} F(x_k)$$

$F(x_k)$ form of the Trapezoidal Rule:

$$F(x_k) = \left(\frac{G}{2} + \frac{C}{\Delta t}\right) x_k + \left(\frac{G}{2} - \frac{C}{\Delta t}\right) x_n + \frac{F'(x_k) + F'(x_n)}{2} - \frac{B(u_{n+1} + u_n)}{2} = 0$$

Implementing Newton's Method

The Jacobian of $F(x_k)$

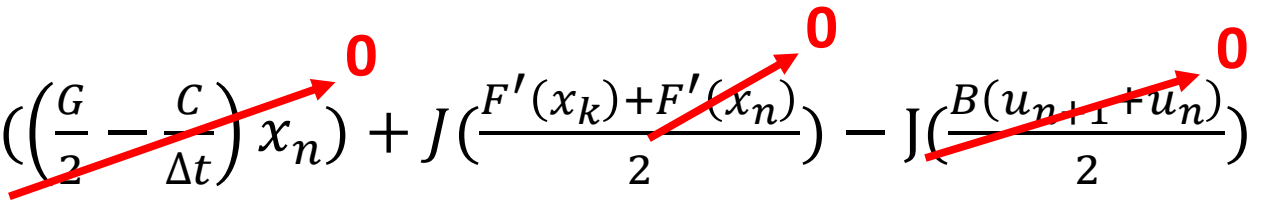
$$J(F(x_k)) = J\left(\left(\frac{G}{2} + \frac{C}{\Delta t}\right)x_k\right) + J\left(\left(\frac{G}{2} - \frac{C}{\Delta t}\right)x_n\right) + J\left(\frac{F'(x_k) + F'(x_n)}{2}\right) - J\left(\frac{B(u_{n+1} + u_n)}{2}\right)$$


$$J(F(x_k)) = \left(\frac{G}{2} + \frac{C}{\Delta t}\right) + \frac{J(F'(x_k))}{2}$$

Note that we need $F'(x)$ and $[J(F(x_k))]^{-1}$ for every guess of x_k .

This means that $F'(x)$, $J(F'(x))$ need to be calculated and $J(F'(x))$ inverted at every guess.

Variable Time Stepping

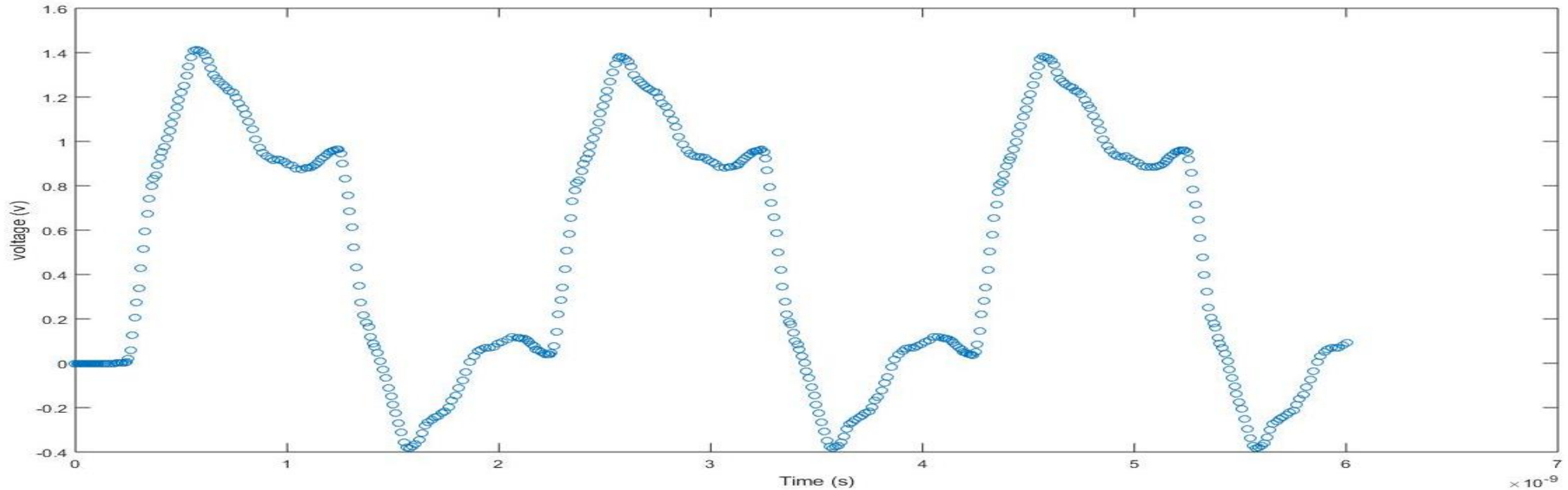



- Large Time Steps when function is smooth
- Small time steps when change is large

Time size depends on Error


- Key Equation:

$$\Delta t_{new} = \min(0.9\sqrt{(\epsilon_{max}/\epsilon)}, \Delta t_{max})$$

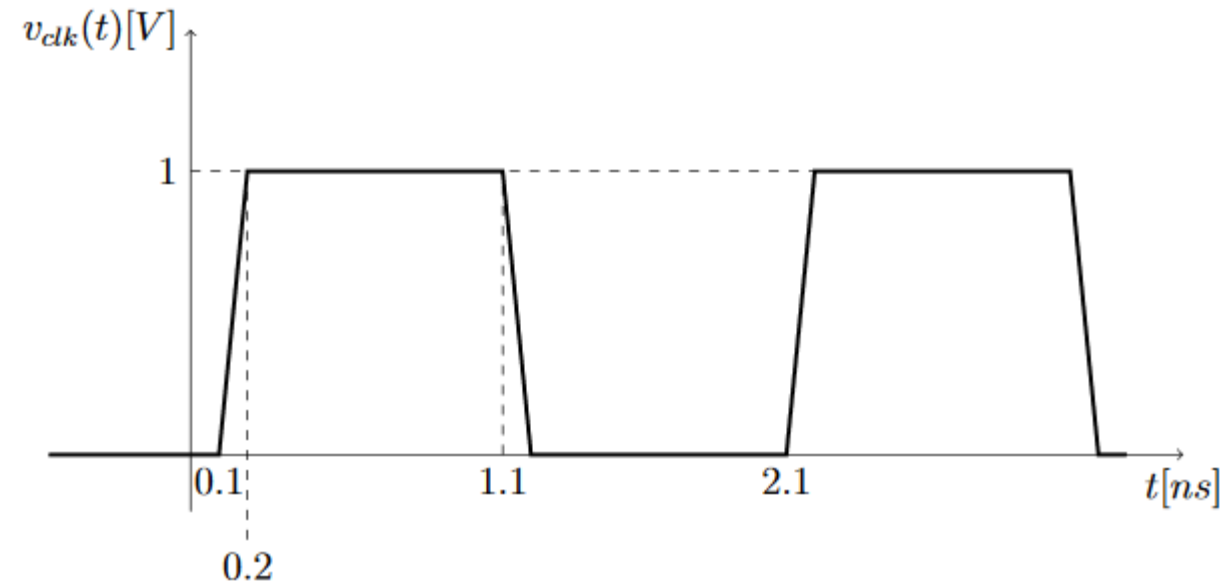
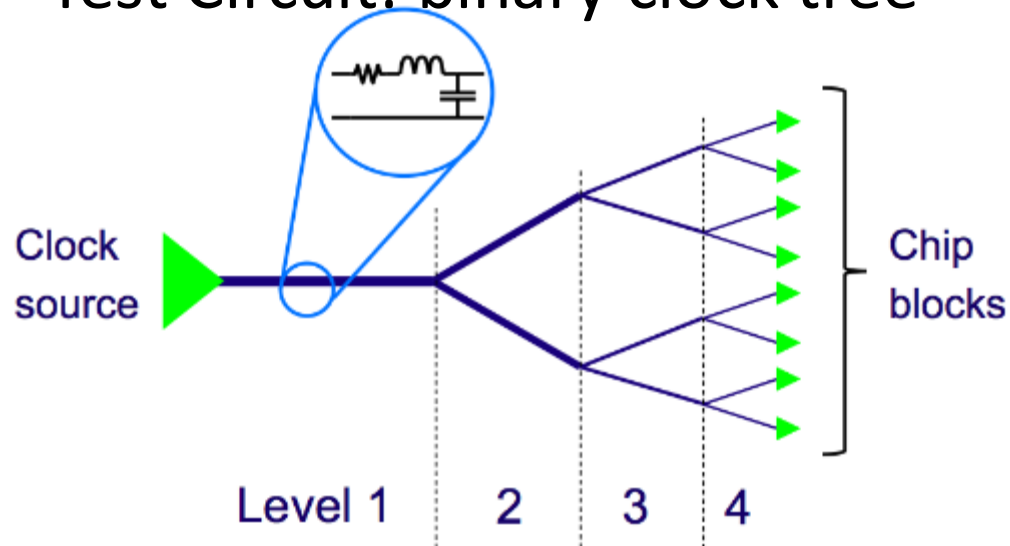
- Error calculates difference in the result of two methods
 - In this case, 1-step trapezoidal and 2-step trapezoidal
- Test Circuit: binary clock tree



Variable Time Stepping

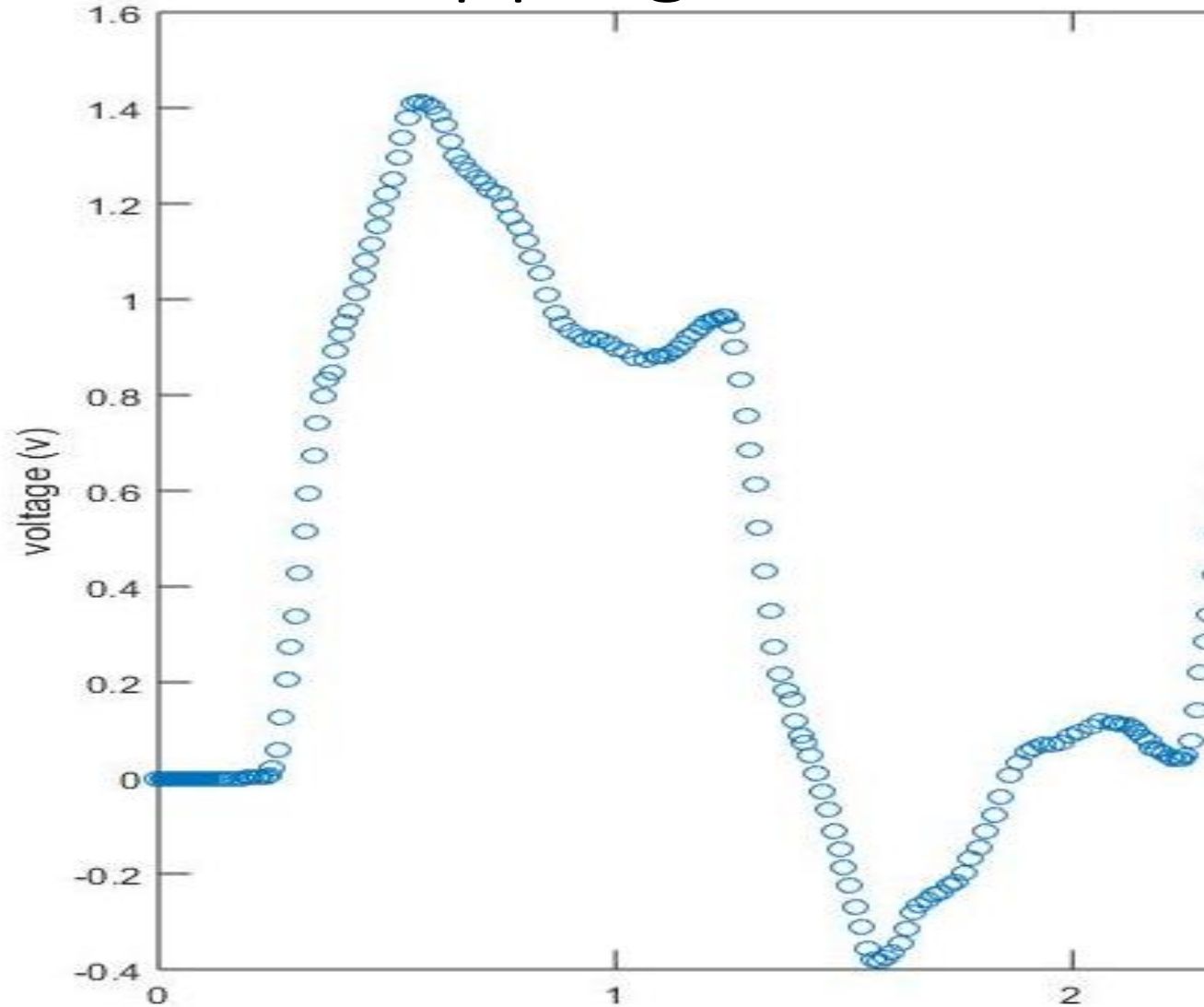

Error of Variable Time Stepping

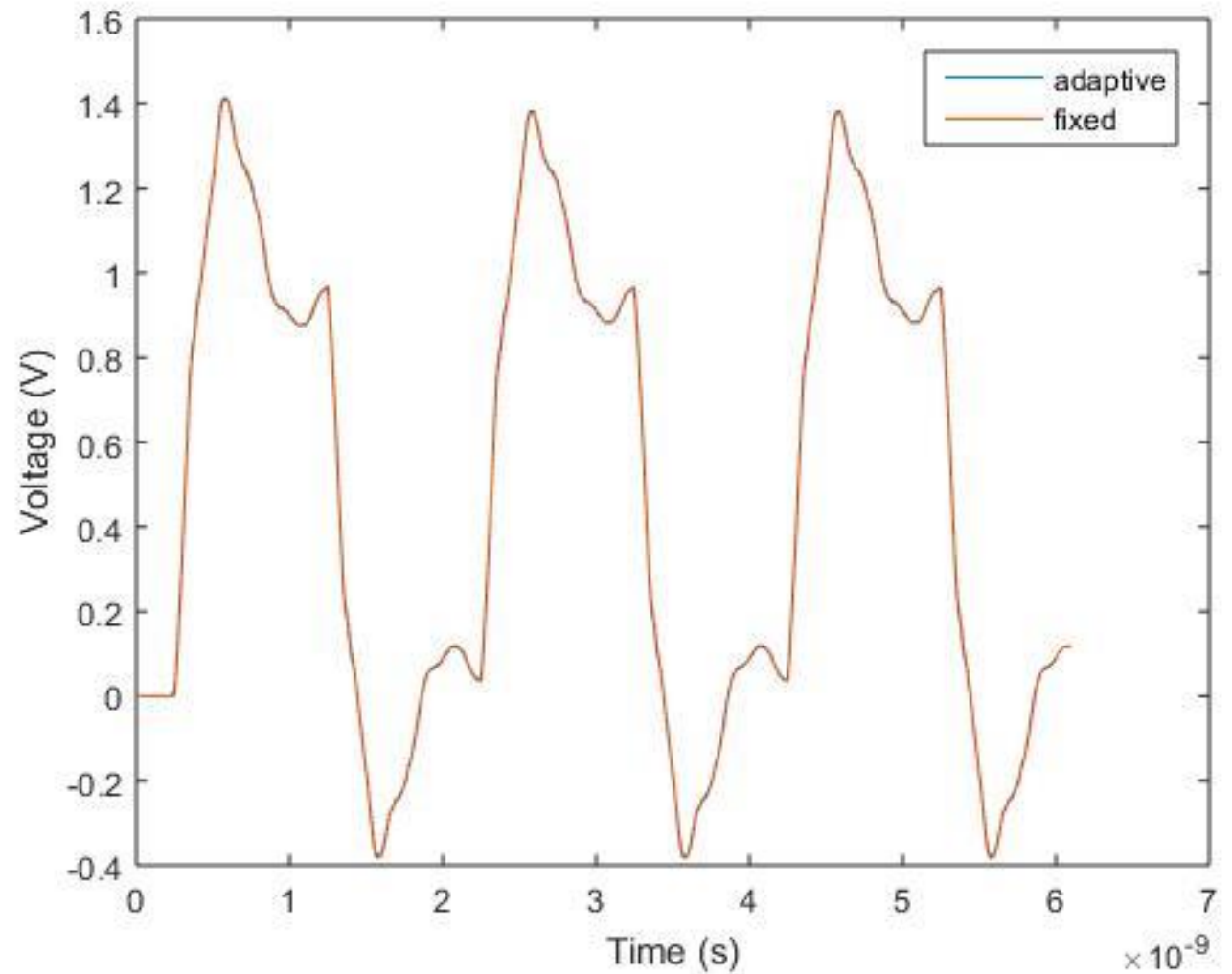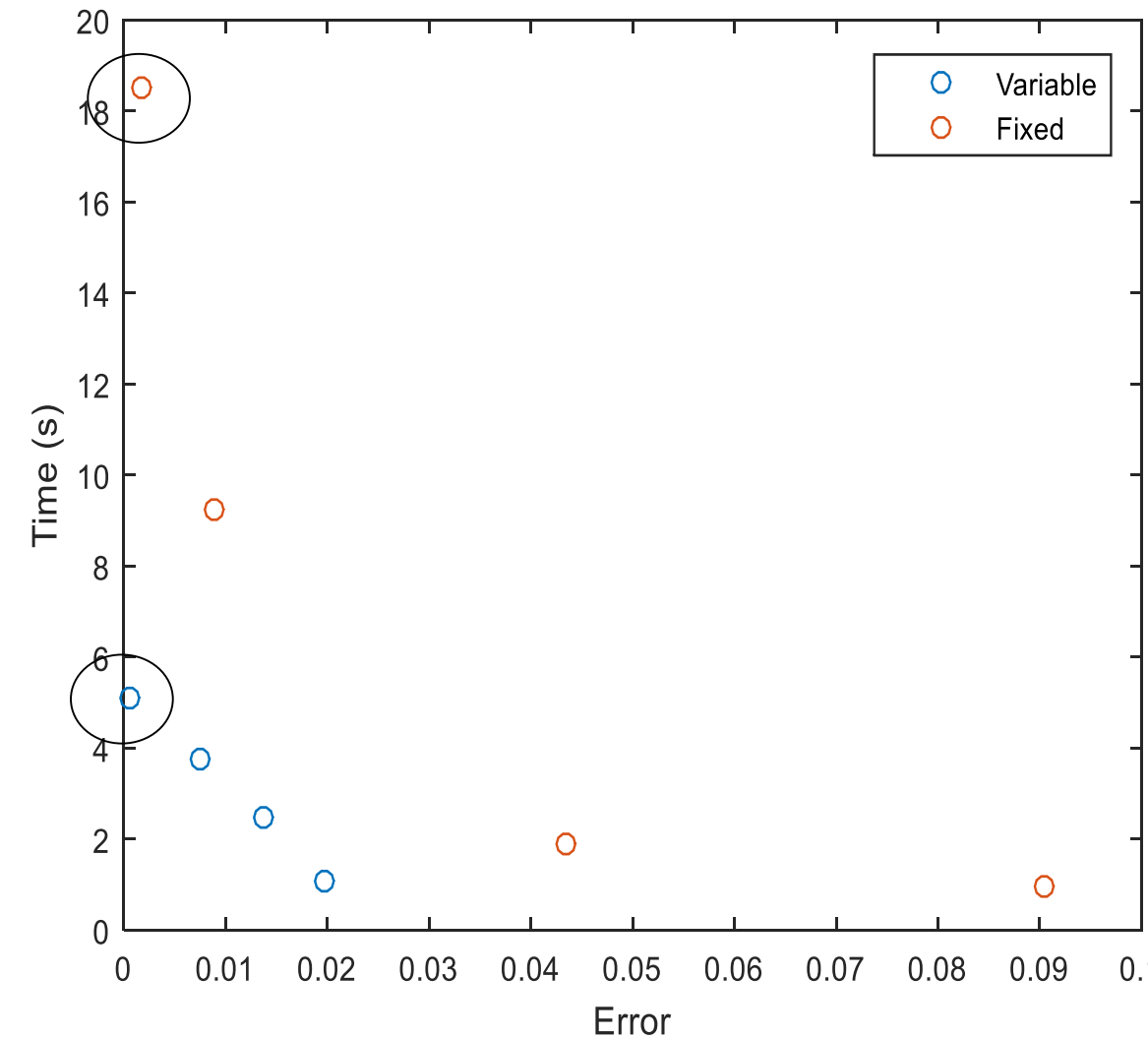


Newton's Method Convergence Strategies


- Large shunt resistors to ground
- Final result of previous time step is used as Newton's Method initial guess of the current time step
- Continuation Method
- Adding time delay to source signal

Some More Improvements

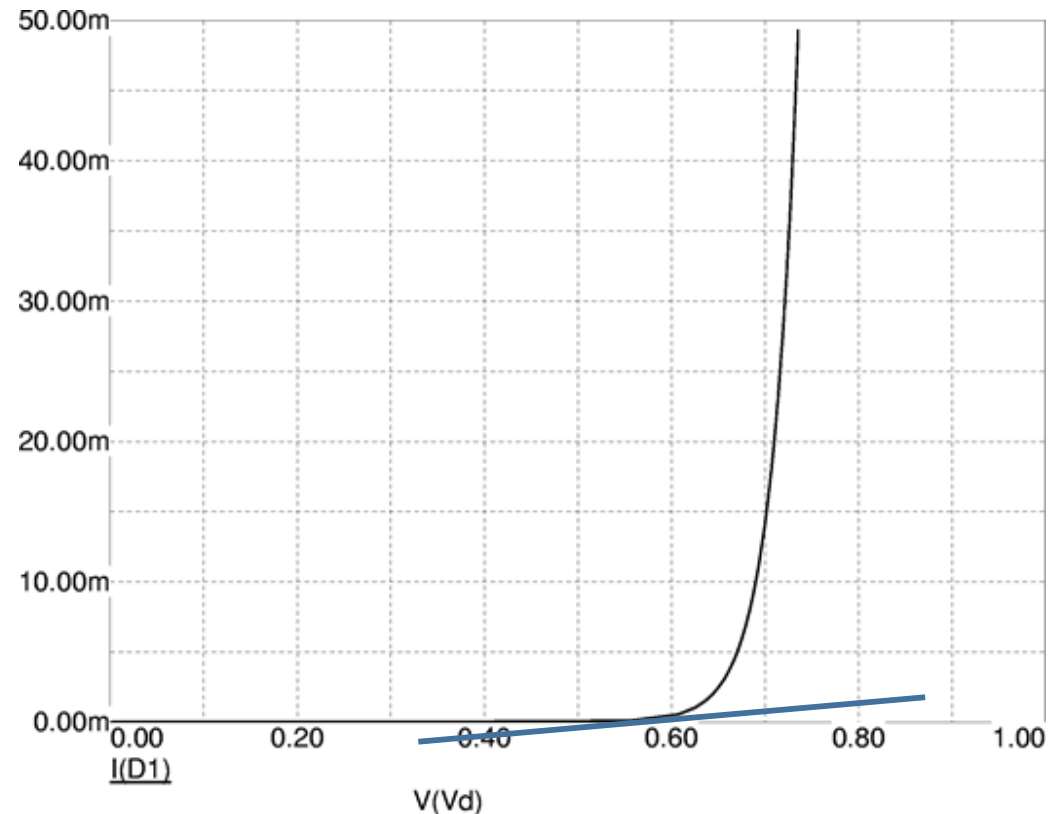- Relaxed Newton's Method convergence minimum error
- Restricted the maximum allowable range for Newton's Method
- $dx = dx_max / \text{norm}(dx) * dx$
- Scale down the amplitudes of incoming signal



Diode Model Equation and Stamps

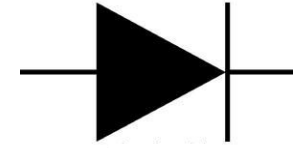

The current for a diode is described by the following equation:

$$i = I_0 \left(e^{\frac{V_+ - V_-}{\eta V_T}} - 1 \right)$$

The stamp follows the format of a non-linear resistor, seen earlier:

$$\begin{array}{c} \textcolor{red}{F'(x)} \\ 1 \\ \vdots \\ n1 \left[\begin{array}{c} I_0 \left(e^{\frac{V_+ - V_-}{\eta V_T}} - 1 \right) \\ \vdots \\ n2 \left[\begin{array}{c} -I_0 \left(e^{\frac{V_+ - V_-}{\eta V_T}} - 1 \right) \\ \vdots \end{array} \right] \end{array} \right] \end{array} \quad \longleftrightarrow \quad \begin{array}{c} \textcolor{blue}{H} \\ n^* \\ \vdots \\ 1 \\ \vdots \\ n1 \left[\begin{array}{c} \vdots \\ 1 \\ \vdots \\ \vdots \end{array} \right] \quad \begin{array}{c} n^* \\ \vdots \\ 1 \\ \vdots \end{array} \left[\begin{array}{c} \vdots \\ I_0 \left(e^{\frac{V_+ - V_-}{\eta V_T}} - 1 \right) \\ \vdots \end{array} \right] \end{array}$$

Jacobian of a Diode Stamp



For $\mathbf{F}'(\mathbf{x})$:

$$\begin{bmatrix} \vdots & & \\ \frac{I_0}{\eta V_T} e^{\frac{V_1 - V_2}{\eta V_T}} & -\frac{I_0}{\eta V_T} e^{\frac{V_1 - V_2}{\eta V_T}} & \\ \vdots & & \\ \dots & -\frac{I_0}{\eta V_T} e^{\frac{V_1 - V_2}{\eta V_T}} & \dots \\ \vdots & \frac{I_0}{\eta V_T} e^{\frac{V_1 - V_2}{\eta V_T}} & \vdots \end{bmatrix}$$



For $\mathbf{g}(\mathbf{x})$:

$$\begin{array}{cc} n_1 & n_2 \\ \left[\frac{\partial i_D}{\partial v} \right] & -\frac{\partial i_D}{\partial v} \\ & J_g \\ n_1 & \left[\begin{array}{cc} +1 & \end{array} \right] \\ n_2 & \left[\begin{array}{cc} -1 & \end{array} \right] \\ & H \quad g \end{array} \begin{bmatrix} i_D \end{bmatrix}$$


Diode Test 1: Half Wave Rectifier

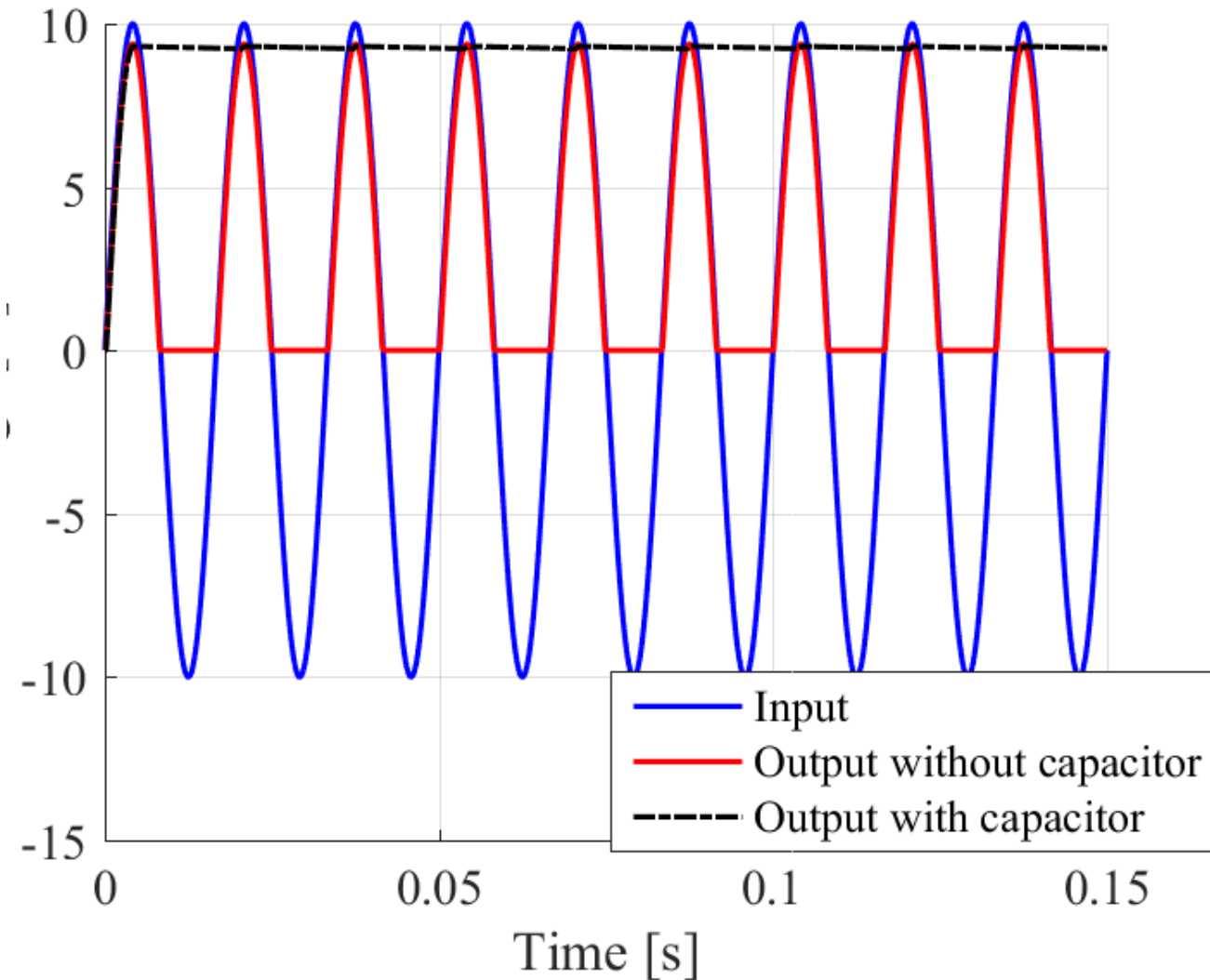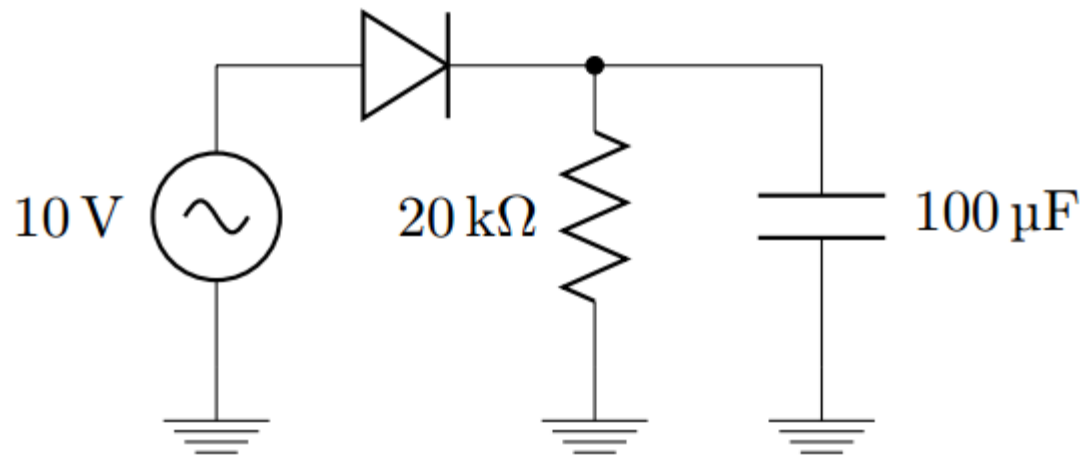

Diode Test 2– Bridge Rectifier

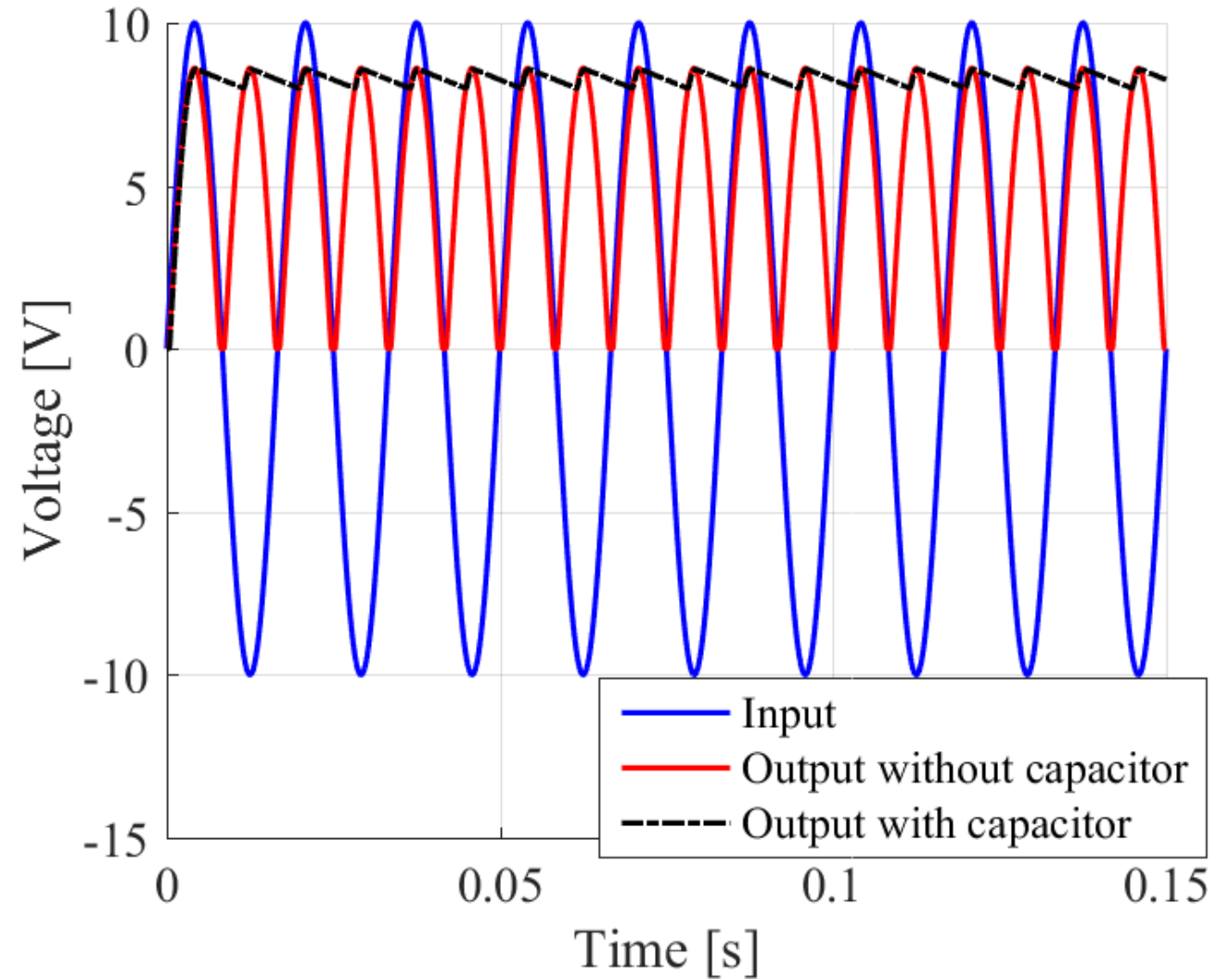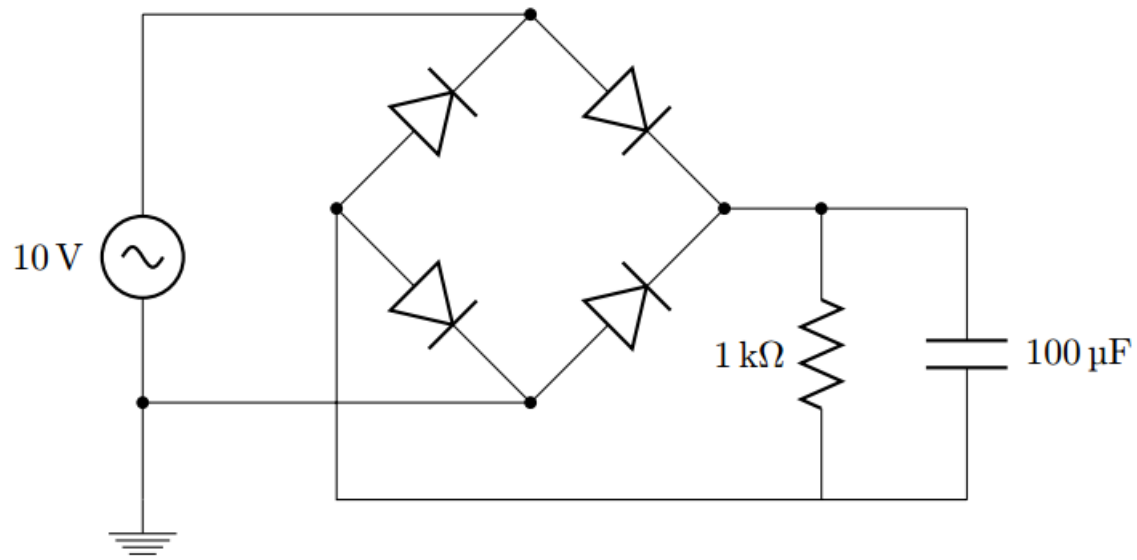

Transistor Model Equations

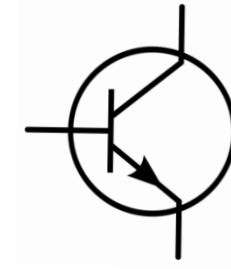

- Ebers-Moll BJT model
 - Simpler to implement than others (e.g. Gummel-Poon)
- From KCL:


$$i_F = I_{Se} (e^{v_{be}/V_{Te}} - 1)$$

$$i_R = I_{Sc} (e^{v_{bc}/V_{Tc}} - 1)$$


$$i_b = (1 - \alpha_F)i_F + (1 - \alpha_R)i_R$$

$$i_c = \alpha_F i_F - i_R$$

$$i_e = -i_F + \alpha_R i_R$$

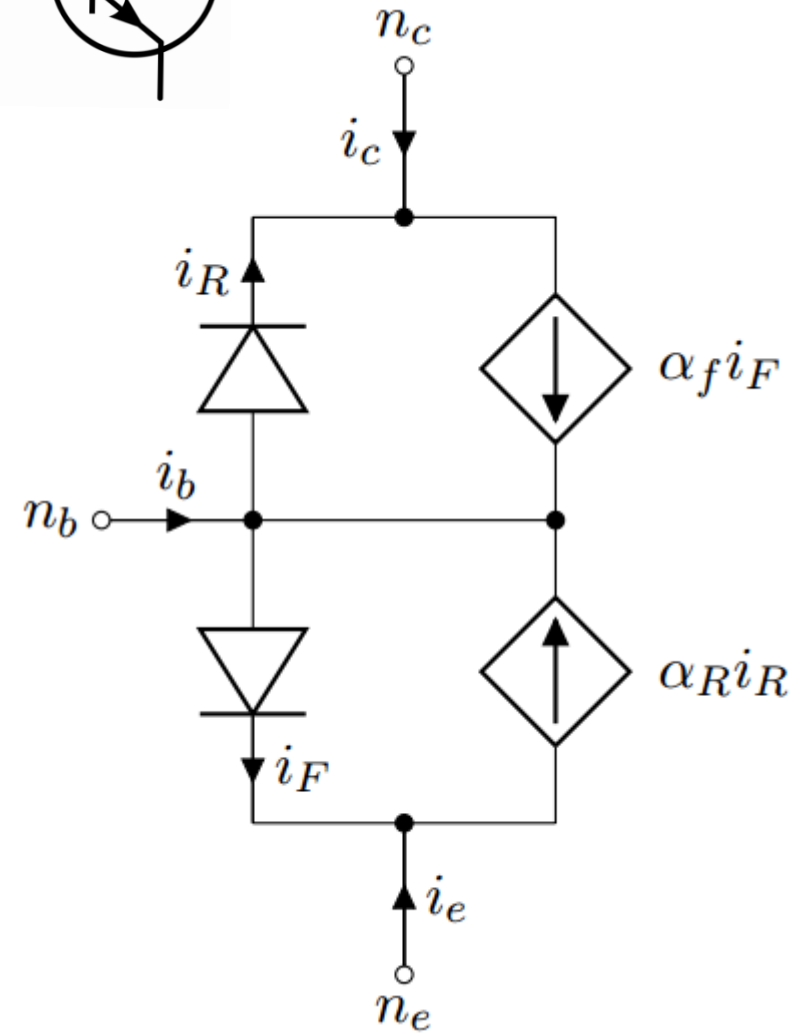

Transistor Stamp


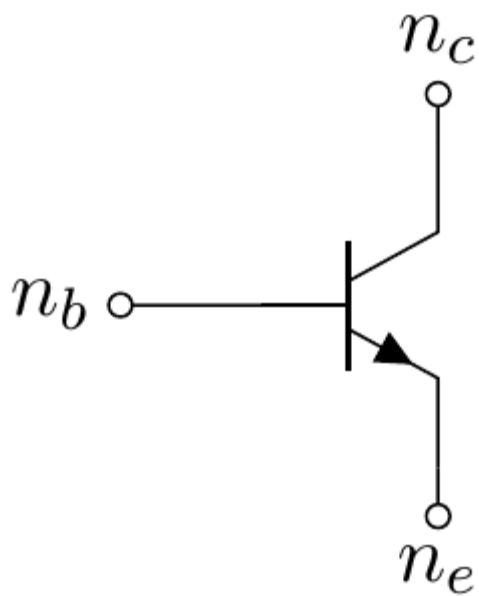


$$\begin{array}{c} n_b \\ n_c \\ n_e \end{array} \begin{bmatrix} (1 - \alpha_F) & (1 - \alpha_R) \\ \alpha_F & -1 \\ -1 & \alpha_R \end{bmatrix} \begin{bmatrix} i_F \\ i_R \end{bmatrix}$$


H
 g

$$\begin{array}{ccc} & n_c & n_b & n_e \\ \begin{bmatrix} 0 & \frac{\partial i_F}{\partial v} & -\frac{\partial i_F}{\partial v} \\ -\frac{\partial i_R}{\partial v} & \frac{\partial i_R}{\partial v} & 0 \end{bmatrix} & & \\ & J_g & & \end{array}$$


Transistor Testing – CE Amplifier

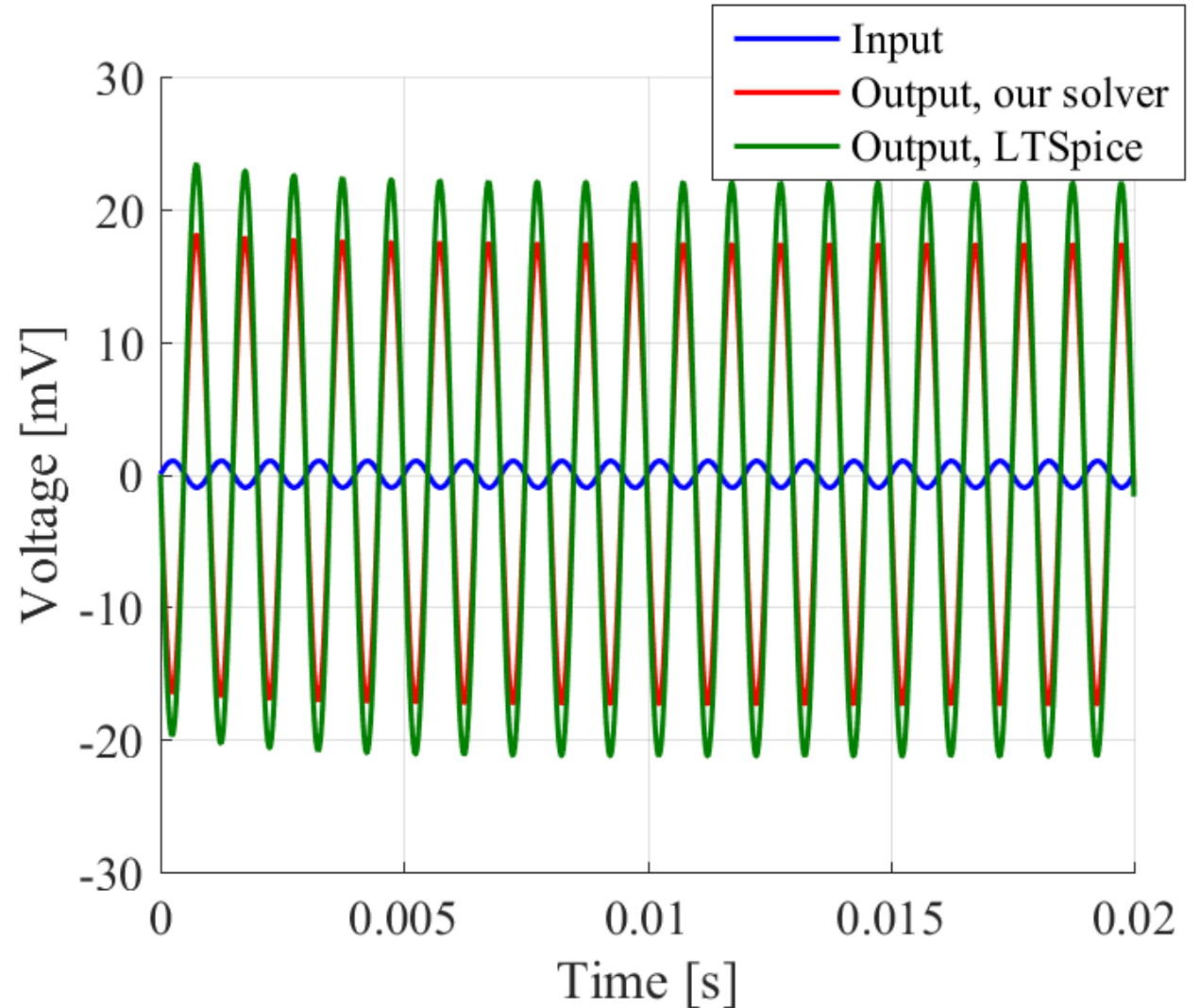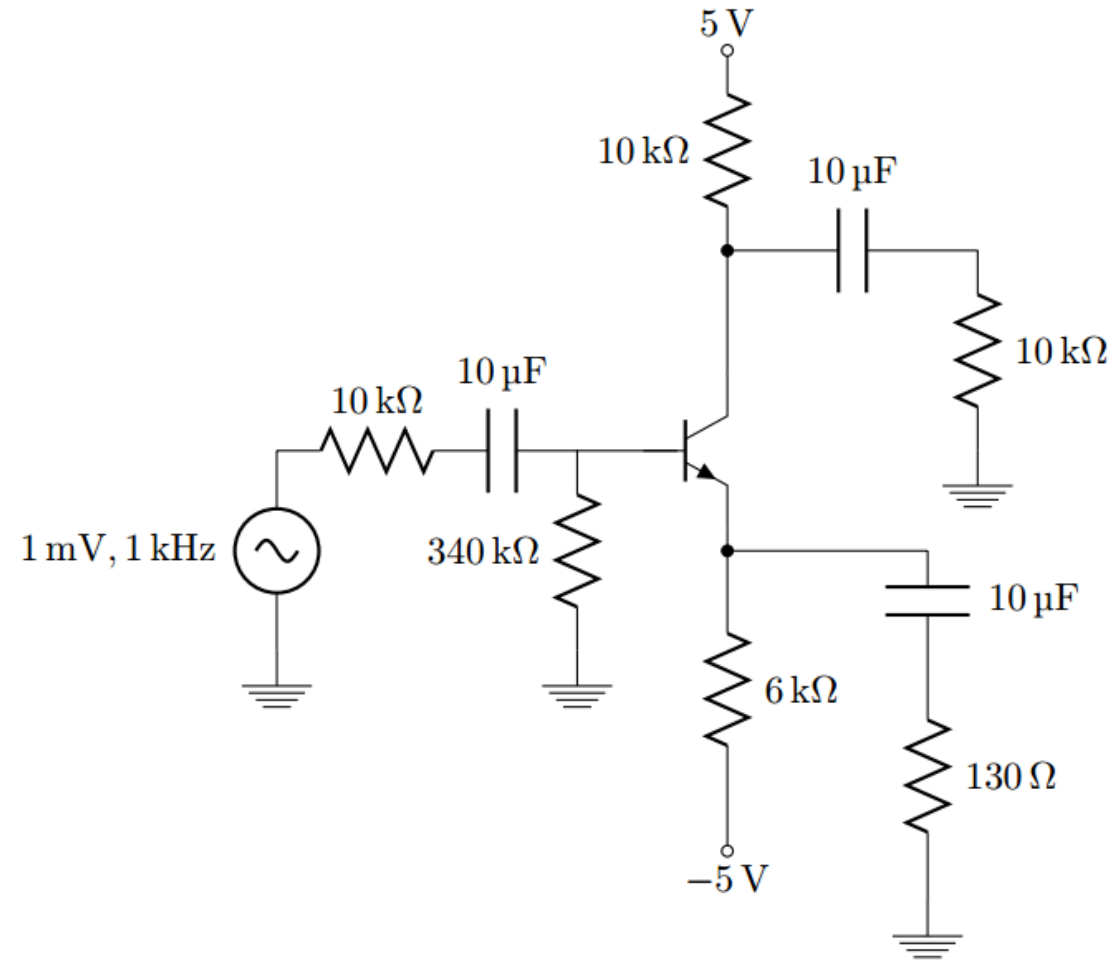

Guitar Effect 1: Tube Screamer Circuit



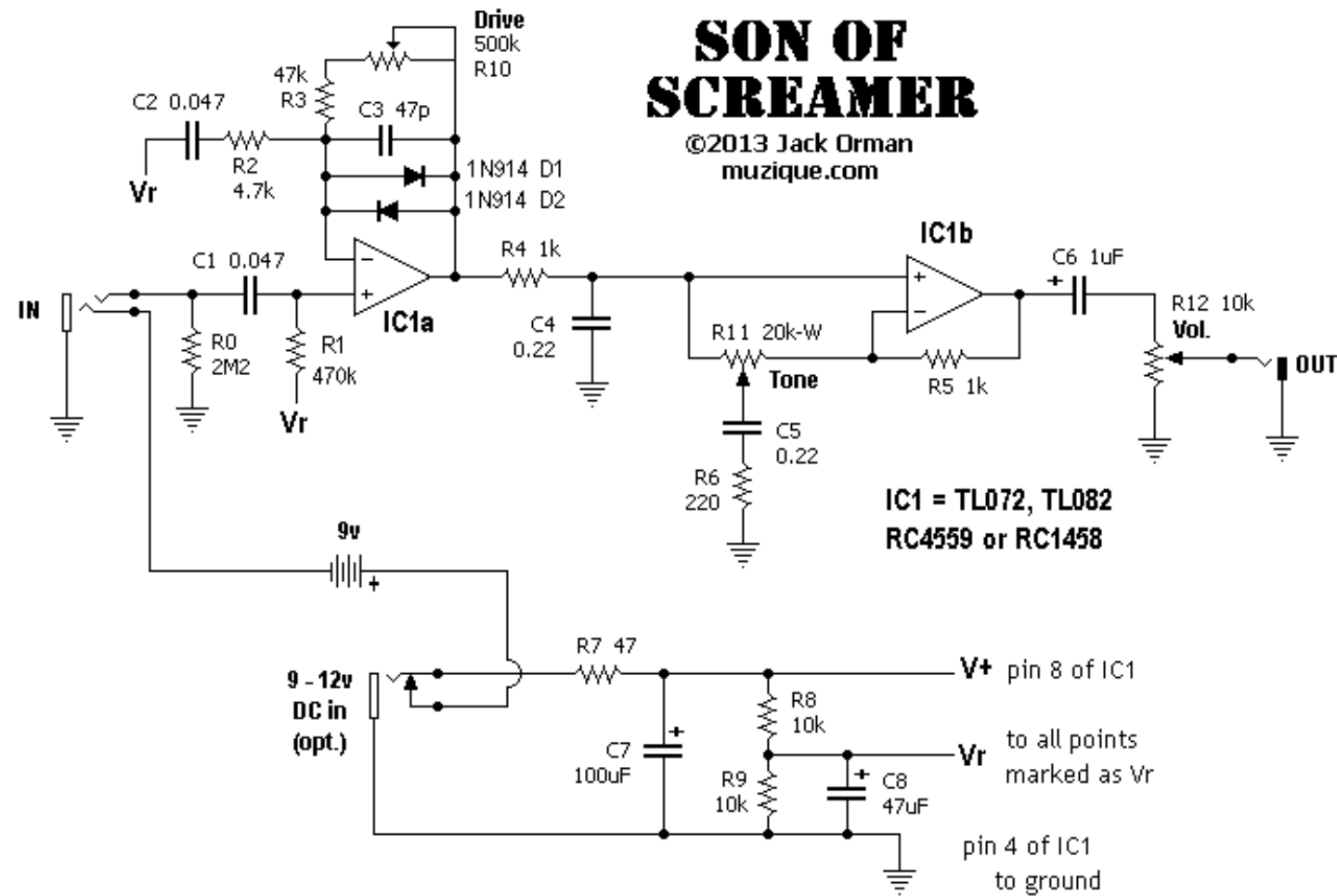


Tube Screamer Input vs. Output

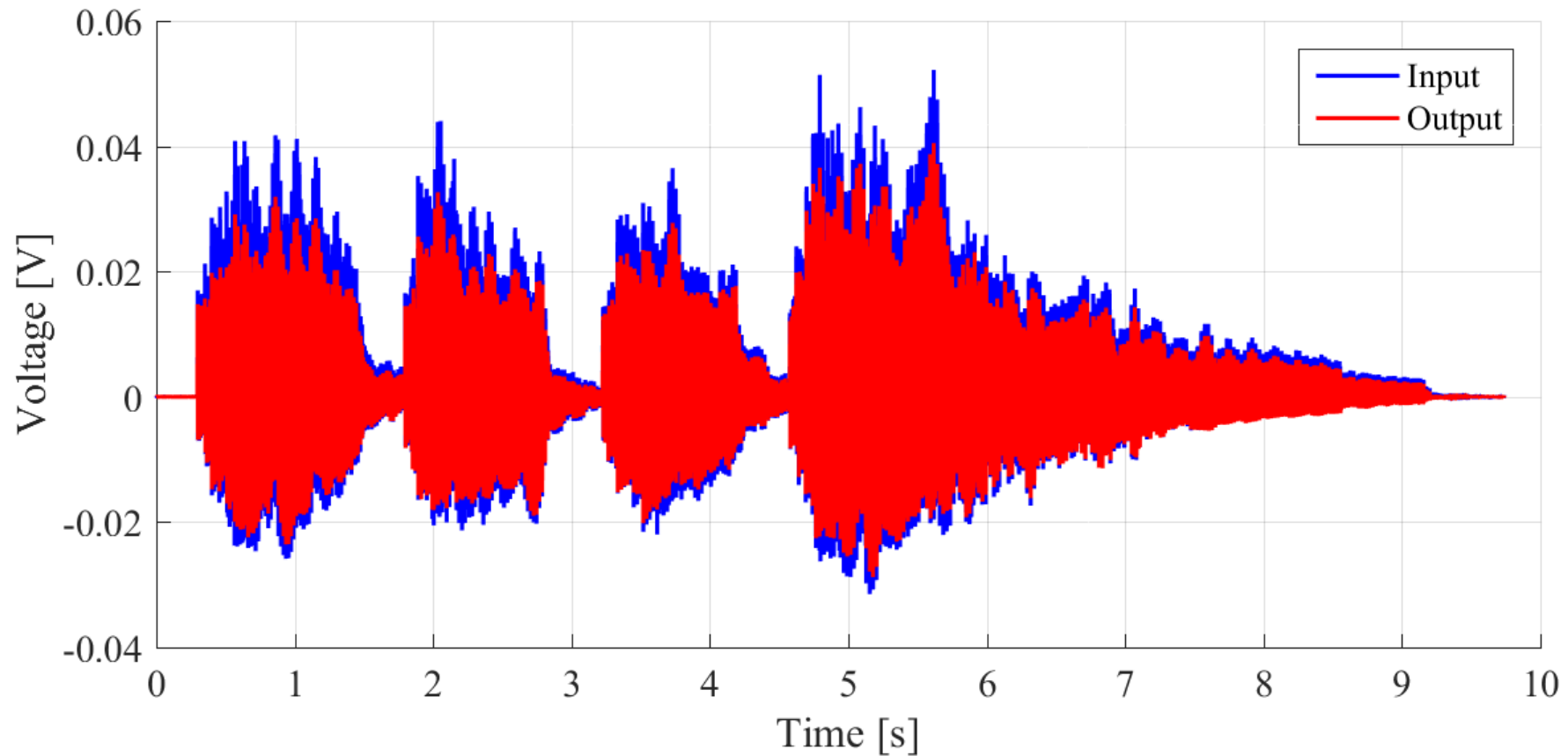

Guitar Effect 2: Fuzz Effect

Iteration	1	2	3	4	5	6
Node 3 Voltage	4.2908	4.2908	4.2907	4.2901	4.2567	NaN
Node 4 Voltage	4.8088	4.7736	4.7083	4.1638	-29.2446	NaN

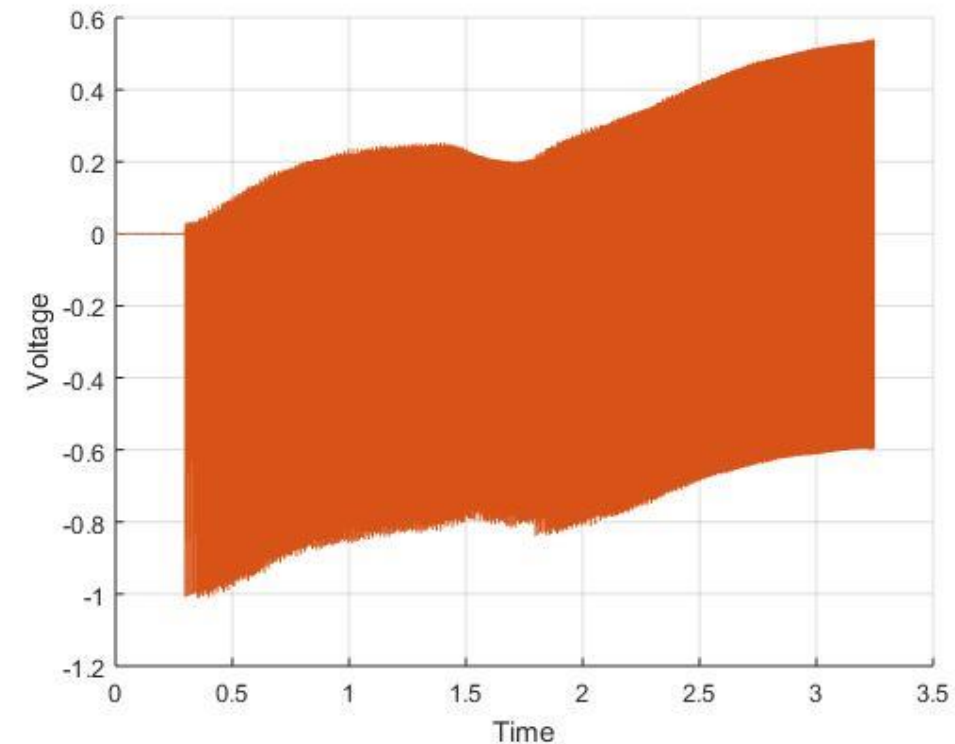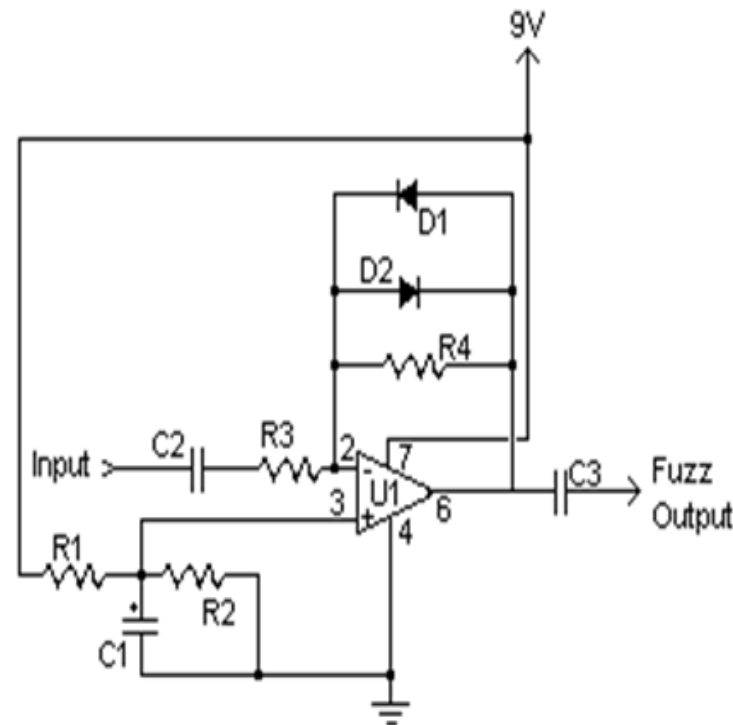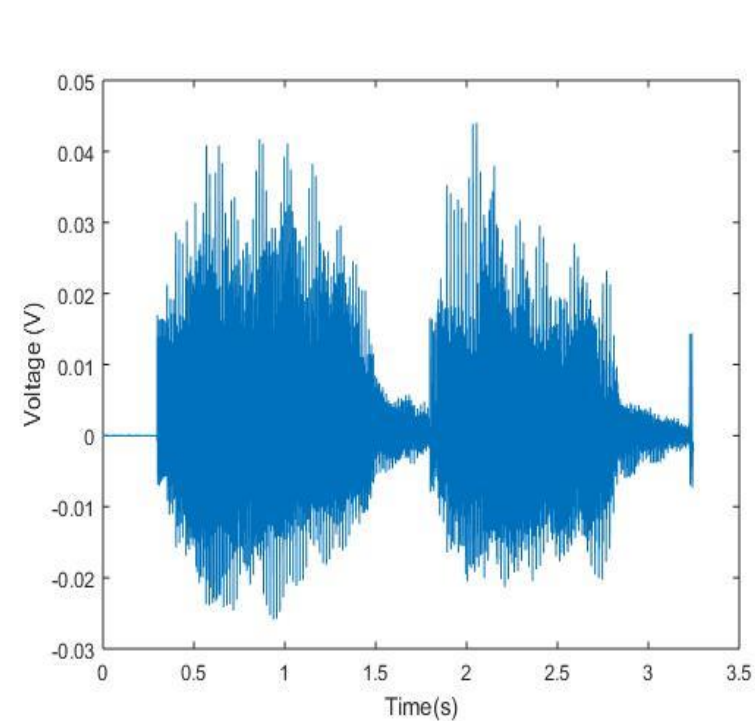

Insights

- Diodes
 - Either the current through the diode becomes unmanageably large, which produces a singular (exceeding precision) inverse-Jacobian, or becomes a poorly scaled non-invertible Jacobian
- Transistors
 - Ebers-Moll model consists of diodes: the problems that are applicable to diodes are also applicable to transistors.
 - A circuit that contains more than one non-linear element (Fuzz Box) becomes very sensitive to voltage, the exponential characteristics cascades, which is harder to control.
- Modelling
 - Although the integration of both methods was depicted as simply integrating two while loops, it still required to reevaluate, by hand, the form of the equations within
 - The error obtained when comparing the variable time step to fixed is smaller, and also computationally faster

Improvements

- Try MOSFET instead of BJT since its I-V curve is quadratic
- Can use algorithm to improve shunt resistor method (Gmin stepping)
- The sensitivity of the diodes may have been manageable if we had time to integrate the variable time stepping
- Scaling units of the voltages, currents, and circuit elements

Questions?

Thank you for your time!

Result

